

Computer Architecture Experiment

Topic 2. 5-stage CPU executing in pipeline

浙江大学计算机学院

陈文智、王总辉

{chenwz, zhwang}@zju.edu.cn



- ftp://10.214.50.74:1021
- 2014_arc_course/2014_arc_course, 只读, 用来下载课件
- 2014_arc_ug_up/2014_arc_ug_up, 可读写, 上传体系结构作业及报告, 每个人都已建好目录



Outline

- **Experiment Purpose**
- **Experiment Task**
- **Basic Principle**
- **Operating Procedures**
- **Precaution**
- **Checkpoints**



Experiment Purpose

- Understand **the principles of Pipelined CPU**
- Understand **the basic units of Pipelined CPU**
- Understand **the working flow of 5-stages**
- Master **the method of simple Pipelined CPU**
- master methods of **program verification of simple Pipelined CPU**

Experiment Task




- Design the **CPU ALU**
- Design the **CPU Controller**
- Based on the CPU Controller, Design the **Datapath of 5-stages Pipelined CPU**
 - 5 Stages
 - Register File
 - Memory (Instruction and Data)
 - other basic units
- **Verify the Pp. CPU with program** and observe the execution of program


Comparison of three CPUs' work




Simple-Cycle CPU

 


Multiple-Cycle CPU

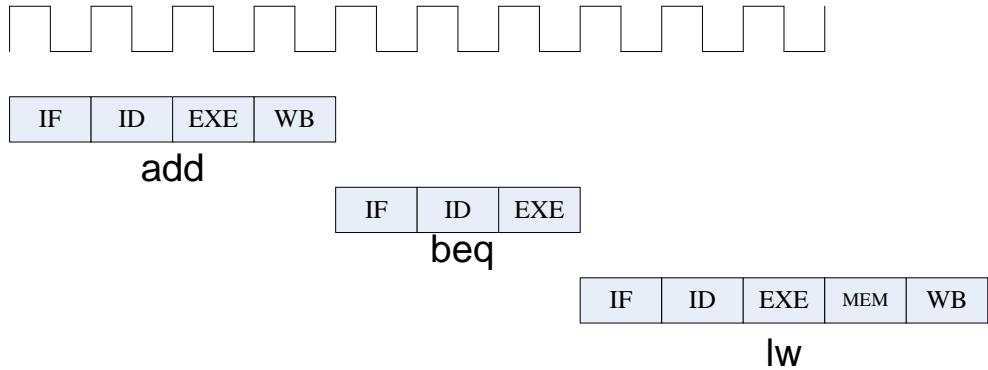


Pipelined CPU

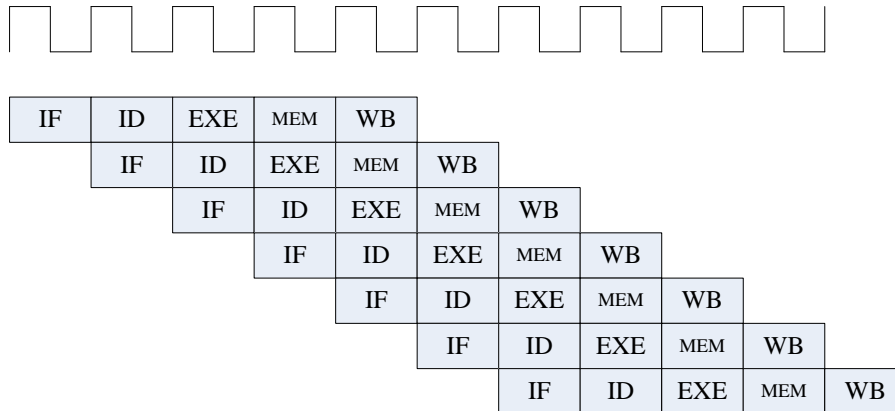

Datapath of 5-stages Pipelined CPU

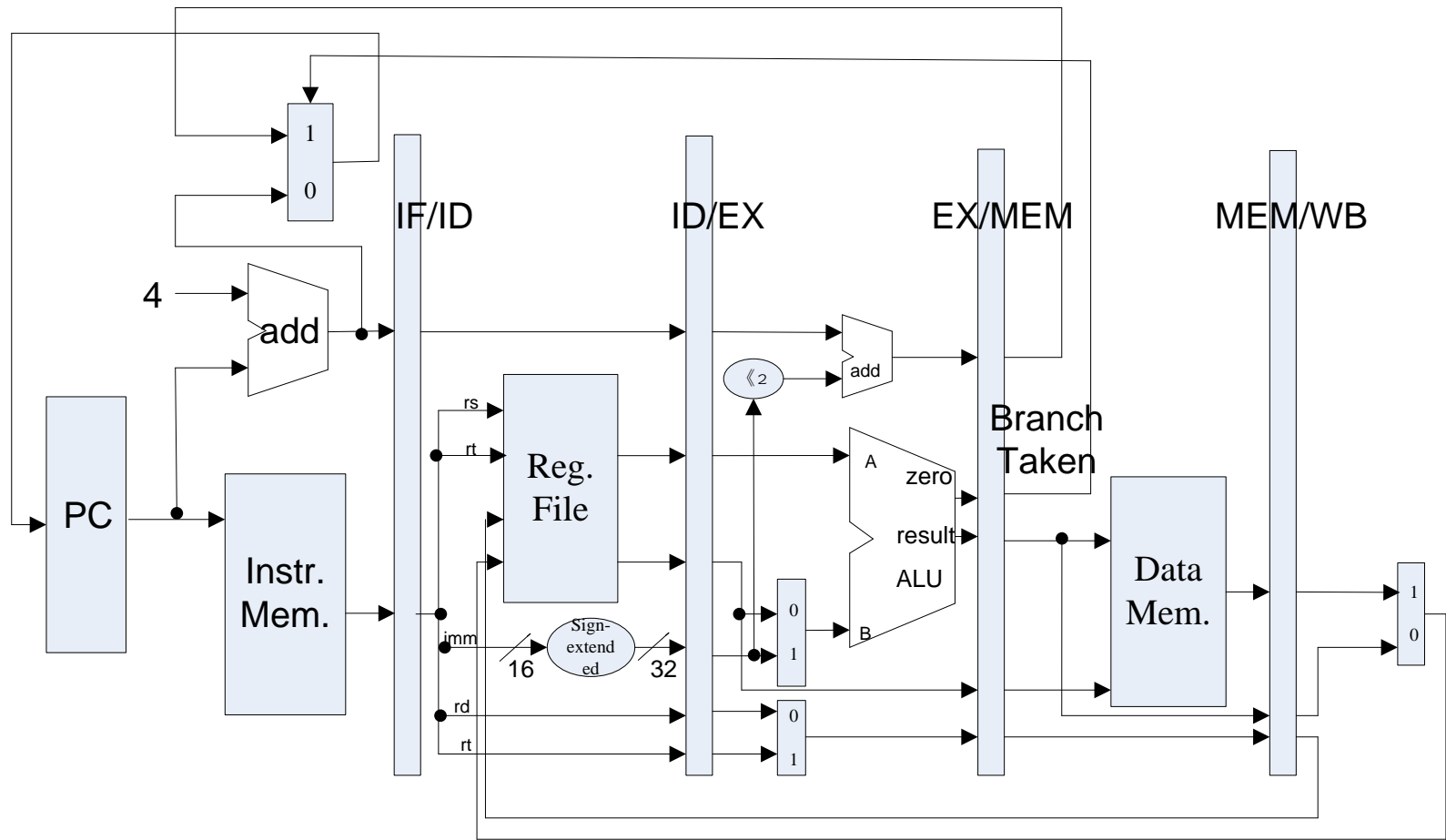

The principle of Multiple-cycle CPU

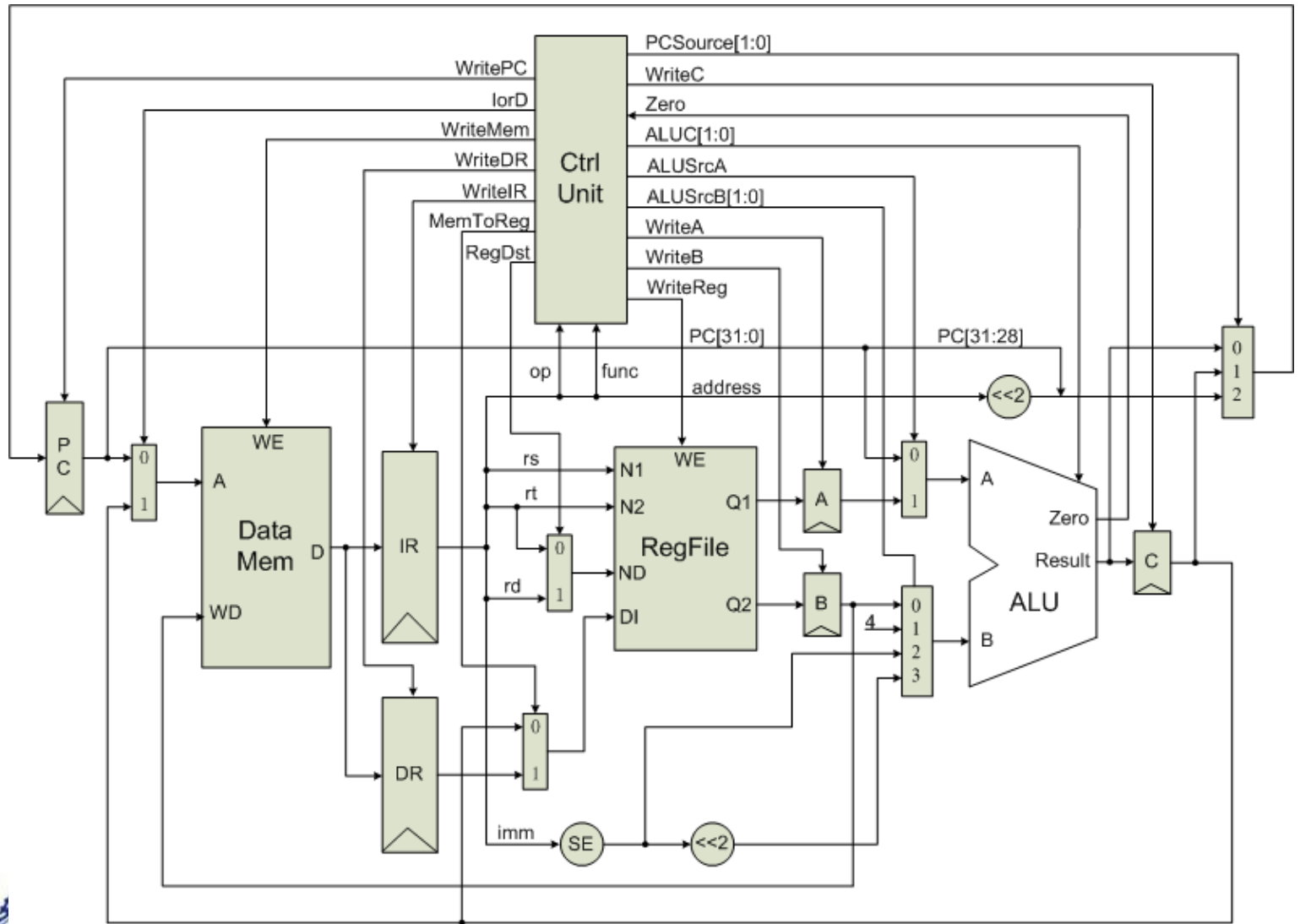


Structural hazards — resource conflicts



- **Structural hazards arise from resource conflicts when the hardware cannot support all possible combinations of instructions in simultaneous overlapped execution.**
 - Memory conflicts
 - Register File conflicts
 - Other units conflicts

How to resolve Structural hazards

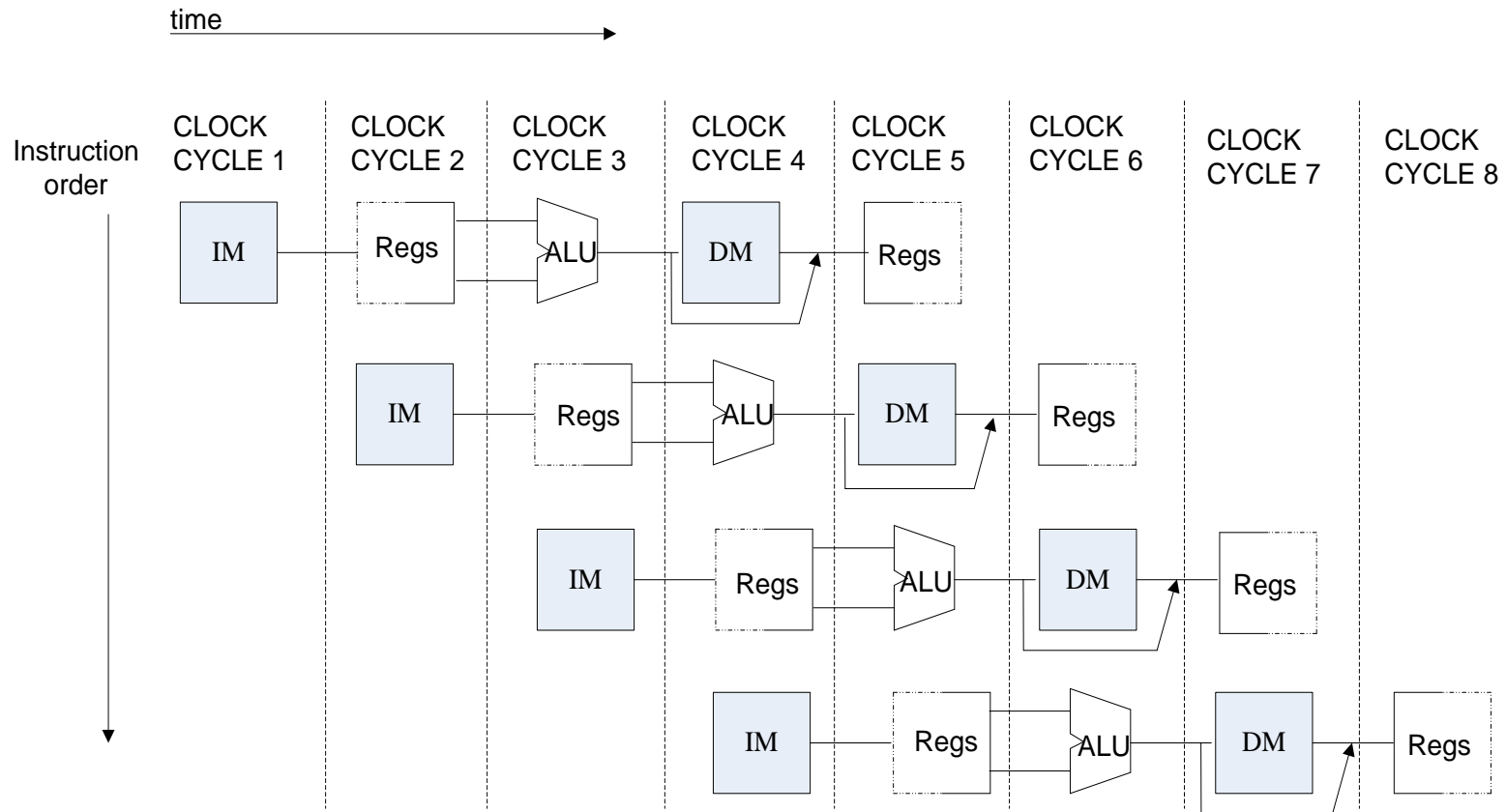



Design of ALU and CU of Pipelined CPU

- **Design the ALU**
- **Design the Control Unit (CPU Controller)**
- **Note:**
 - Use all MIPS instructions defined in macro.vh file !
- **Our Ultimate Task in the Course:**
 - ✓ Design a Pipelined CPU support execution **31 MIPS Instructions (show in next table)**



Output of CPU Controller

	Output Signal	Meaning When 1	Meaning When 0
1	Cu_branch	Branch Instr.	Non-Branch Instr.
2	Cu_shift	sa	Register data1
3	Cu_wmem	Write Mem.	Not Write Mem.
4	Cu_Mem2Reg	From Mem. To Reg	From ALUOut To Reg
5	Cu_sext	Sign-extend the imm.	No sign extended the imm.
6	Cu_aluc	ALU Operation	
7	Cu_aluimm	Imm.	Register data2
8	Cu_wreg	Write Reg.	Not Write Reg.
9	Cu_regrt	rt	rd

Pipelined CPU supporting execution of 31 MIPS instructions



MIPS Instructions								
Bit #	31..26	25..21	20..16	15..11	10..6	5..0	Operations	
R-type	op	rs	rt	rd	sa	func		
add	000000	rs	rt	rd	00000	100000	rd = rs + rt; with overflow	PC+=4
addu		rs	rt	rd	00000	100001	rd = rs + rt; without overflow	PC+=4
sub		rs	rt	rd	00000	100010	rd = rs - rt; with overflow	PC+=4
subu		rs	rt	rd	00000	100011	rd = rs - rt; without overflow	PC+=4
and		rs	rt	rd	00000	100100	rd = rs & rt;	PC+=4
or		rs	rt	rd	00000	100101	rd = rs rt;	PC+=4
xor		rs	rt	rd	00000	100110	rd = rs ^ rt;	PC+=4
nor		rs	rt	rd	00000	100111	rd = ~(rs rt);	PC+=4
slt		rs	rt	rd	00000	101010	if(rs < rt)rd = 1; else rd = 0; <(signed)	PC+=4
sltu		rs	rt	rd	00000	101011	if(rs < rt)rd = 1; else rd = 0; <(unsigned)	PC+=4
sll		00000	rt	rd	sa	000000	rd = rt << sa;	PC+=4
srl		00000	rt	rd	sa	000010	rd = rt >> sa (logical);	PC+=4
sra		00000	rt	rd	sa	000011	rd = rt >> sa (arithmetic);	PC+=4
sllv		rs	rt	rd	00000	000100	rd = rt << rs;	PC+=4
srlv		rs	rt	rd	00000	000110	rd = rt >> rs (logical);	PC+=4
srav		rs	rt	rd	00000	000111	rd = rt >> rs(arithmetic);	PC+=4
jr	rs	00000	00000	00000	001000		PC=rs	

Pipelined CPU supporting execution of 31 MIPS instructions



MIPS Instructions							
Bit #	31..26	25..21	20..16	15..11	10..6	5..0	Operations
I-type	op	rs	rt	immediate			
addi	001000	rs	rt	imm			rt = rs + (sign_extend)imm; with overflow PC+=4
addiu	001001	rs	rt	imm			rt = rs + (sign_extend)imm; without overflow PC+=4
andi	001100	rs	rt	imm			rt = rs & (zero_extend)imm; PC+=4
ori	001101	rs	rt	imm			rt = rs (zero_extend)imm; PC+=4
xori	001110	rs	rt	imm			rt = rs ^ (zero_extend)imm; PC+=4
lui	001111	00000	rt	imm			rt = imm * 65536; PC+=4
lw	100011	rs	rt	imm			rt = memory[rs + (sign_extend)imm]; PC+=4
sw	101011	rs	rt	imm			memory[rs + (sign_extend)imm] <-- rt; PC+=4
beq	000100	rs	rt	imm			if (rs == rt) PC+=4 + (sign_extend)imm <<2; PC+=4
bne	000101	rs	rt	imm			if (rs != rt) PC+=4 + (sign_extend)imm <<2; PC+=4
slti	001010	rs	rt	imm			if (rs < (sign_extend)imm) rt = 1 else rt = 0; less than signed PC+=4
sltiu	001011	rs	rt	imm			if (rs < (zero_extend)imm) rt = 1 else rt = 0; less than unsigned PC+=4
J-type	op	address					
j	000010	address					PC = (PC+4)[31..28], address <<2
jal	000011	address					PC = (PC+4)[31..28], address <<2 ; \$31 = PC+4



Register File

- **Register File**
 - Positive edge for transfer data for stages
 - Negative edge for write operation
 - Low level for read operation



Memory

- **Instruction Memory**
 - Single Port Block Memory
 - Read only, Width:32, Depth: 256
 - **Falling** Edge Triggered
- **Data Memory**
 - Single Port Block Memory
 - Read and write, Width:32, Depth: 256
 - **Falling** Edge Triggered



Units of Pipelined-cycle CPU

- **IF Stage (Instr. Mem.)**
- **ID Stage (CPU Ctl. And R.F.)**
- **EX Stage (ALU)**
- **Mem Stage (Data Mem.)**
- **WB Stage**



Pipelined CPU Top Module

```
module top (input wire CCLK, BTN3, BTN2, input wire [3:0]SW, output wire
LED, LCDE, LCDRS, LCDRW, output wire [3:0]LCDDAT);
    assign pc [31:0] = if_npc[31:0];
    if_stage x_if_stage(BTN3, rst, pc, mem_pc, mem_branch, ...
        IF_ins_type, IF_ins_number, ID_ins_type, ID_ins_number);
    id_stage x_id_stage(BTN3, rst, if_inst, if_pc4, wb_destR, ...
        ID_ins_type, ID_ins_number, EX_ins_type, EX_ins_number.);
    ex_stage x_ex_stage(BTN3, id_imm, id_inA, id_inB, id_wreg, ..
        EX_ins_type, EX_ins_number, MEM_ins_type, MEM_ins_number);
    mem_stage x_mem_stage(BTN3, ex_destR, ex_inB, ex_aluR, ...
        MEM_ins_type, MEM_ins_number, WB_ins_type,
WB_ins_number);
    wb_stage x_wb_stage(BTN3, mem_destR, mem_aluR, ...
        WB_ins_type, WB_ins_number, OUT_ins_type, OUT_ins_number);
endmodule
```

Observation Info



- **Input**
 - West Button: Step execute
 - South Button: Reset
 - 4 Slide Button: Register Index
- **Output**
 - 0-7 Character of First line: Instruction Code
 - 8 of First line : Space
 - 9-10 of First line : Clock Count
 - 11 of First line : Space
 - 12-15 of First line : Register Content
 - Second line : “stage name”/number/type
 - stage name: 1-“f”, 2-“d”, 3-“e”, 4-“m”, 5-“w”



Program for verification

Instruction	Bin Code	Address	Inst. Type
lw r1, \$20(r0)	0x8c01_0014	0	6
lw r6, \$21(r0)	0x8c06_0015	1	6
add r3,r0,r0	0x0000_1820	2	1
add r4,r0,r0	0x0000_2020	3	1
add r5,r0,r0	0x0000_2820	4	1
add r2,r2,r1	0x0041_1020	5	1
sub r3, r3, r1	0x0061_1822	6	2
and r4, r4, r1	0x0081_2024	7	3
nor r5, r5, r1	0x00a1_2827	8	5
beq r2, r1, -8	0x1041_fff8	9	8

Precaution



- **1. Add Anti-Jitter and display for “A-F”.**
- **2. Finish the blank.**
- **3. Debug method: Output whatever signal to LCD Display.**
- **4. Understand the principle of pipelined CPU and check the logic of circuit carefully, understand the sample code, then write code and synthesize the project, because it takes you a few minutes...**

Something Important ! ! !



- **The number and type are mean for the instruction which is to be executed in the stage.**
- **How to verify the result? Pls. check the result of WB stage for R-type and LW instructions, while check the result of EXEC stage for BEQ instruction.**
- **Why there are some NONE instructions following BEQ? How many NONE instructions? 3, because the condition of BEQ is generated in MEM stage.**
- **Why use the Reset button to initialize?**
- **Why we should pull the slide button after step execution to refresh the result? And instruction refresh is delayed by 1 clock-cycle? How to refresh automatically?**

Checkpoints



- **CP 1:** Waveform Simulation of 5-stage Pipelined CPU ALU
- **CP 2:** Waveform Simulation of 5-stage Pipelined CPU CU
- **CP 3 (Optional):** Waveform Simulation of 5-stage Pipelined CPU with the verification program
- **CP 4:** FPGA Implementation of 5-stage Pipelined CPU with the verification program



Thanks!